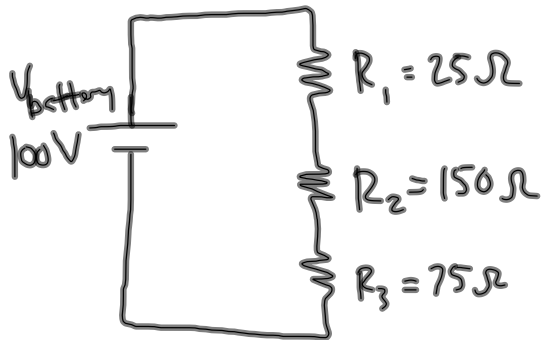


Circuit Practice:find V 's and I 's
of all resistors

$$R_{eq} = R_1 + R_2 + R_3 \\ = 250\Omega$$

$$I_{\text{total}} = \frac{V_{\text{battery}}}{R_{eq}} = \frac{100V}{250\Omega} = 0.4A$$



$$V_1 = I_{\text{total}} R_1 = 10V$$

$$V_2 = I_{\text{total}} R_2 = 60V$$

$$V_3 = I_{\text{total}} R_3 = 30V$$

$$V_1 = 10V$$

$$V_2 = 60V$$

$$V_3 = 30V$$

$$I_1 = 0.4A$$

$$I_2 = 0.4A$$

$$I_3 = 0.4A$$


Steps:

1. Find equivalent resistance of the circuit.


2. Calculate total current from $I_{\text{total}} = \frac{V_{\text{battery}}}{R_{\text{eq}}}$.

3. Work backwards to find individual voltage drops and currents.

Circuit Practice 5.10.12 Honors Physics

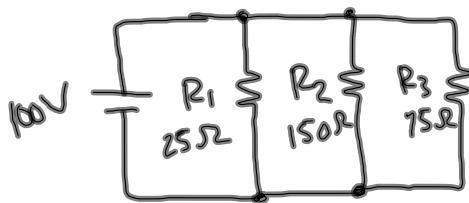

Find I 's and
 V 's of
resistors

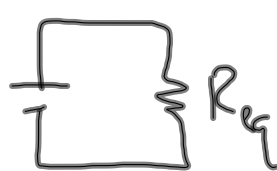


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = 16.67 \Omega$$

$$\left(\left(\frac{1}{25} \right) + \left(\frac{1}{150} \right) + \left(\frac{1}{75} \right) \right)^{-1}$$

$$I_{total} = \frac{V_{battery}}{R_{eq}} = 5.998 A$$

$$V_1 = V_2 = V_3 = 100 V$$



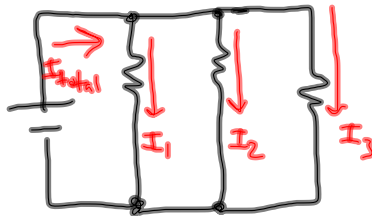


$$I_1 = \frac{V_1}{R_1} = 4 A$$



$$I_2 = \frac{V_2}{R_2} = 0.67 A$$

$$I_3 = \frac{V_3}{R_3} = 1.33 A$$

Circuit Practice 5.10.12 Honors Physics

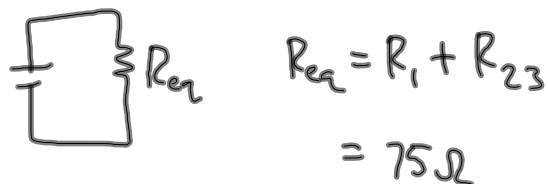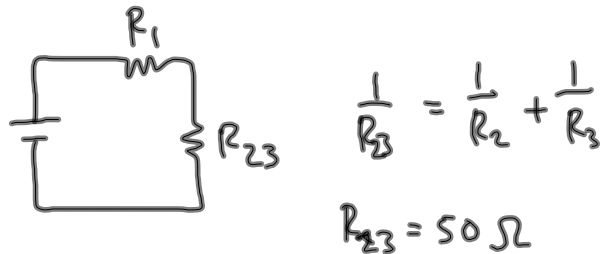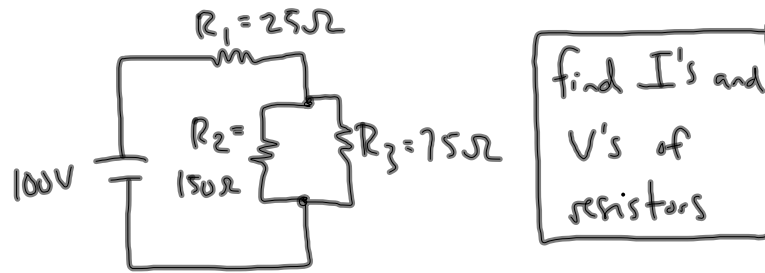

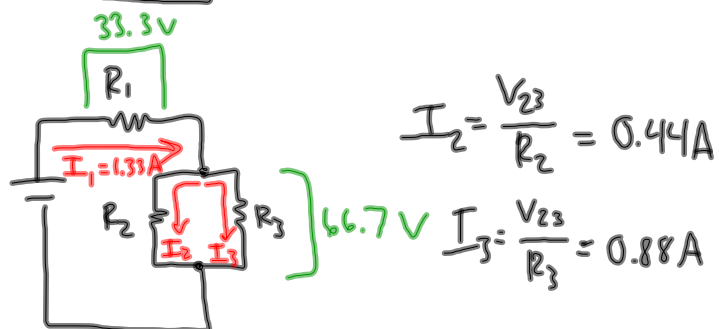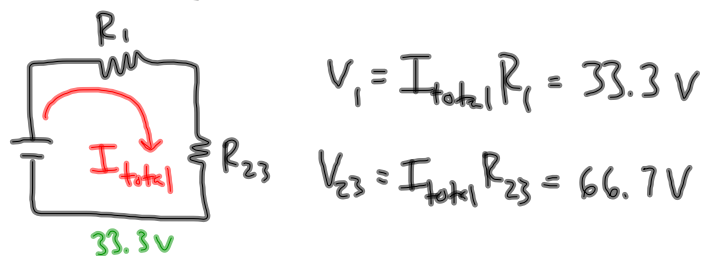
$$I_{total} = \frac{V_{battery}}{R_{eq}} = \frac{100V}{75\Omega} = 1.33A$$




$$V_1 = 33.3V \quad V_2 = 66.7V \quad V_3 = 66.7V$$

$$I_1 = 1.33A \quad I_2 = 0.44A \quad I_3 = 0.88A$$

Circuit Practice 5.10.12 Honors Physics

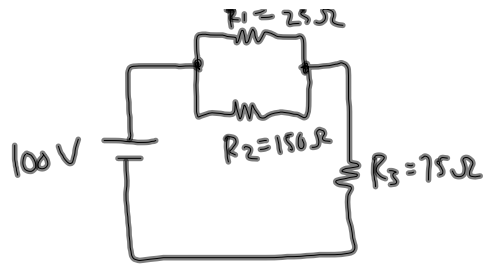

find all V's
and I's

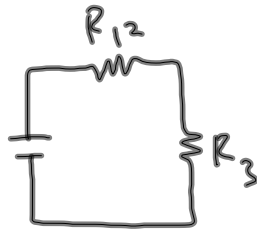

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_{12} = 21.4\Omega$$



$$R_{eq} = R_{12} + R_3$$


$$= 96.1\Omega$$
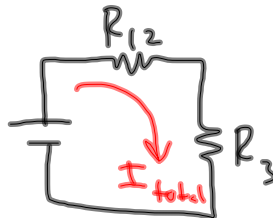
$$I_{total} = \frac{V_{battery}}{R_{eq}} = 1.04A$$



$$V_{12} = I_{total} R_{12} = 22.2V$$

$$V_3 = I_{total} R_3 = 77.8V$$

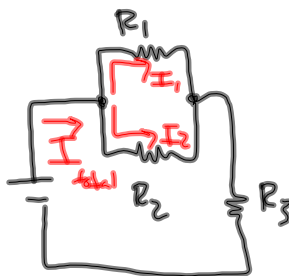

$$I_1 = \frac{V_{12}}{R_1} = 0.88A$$

$$I_2 = \frac{V_{12}}{R_2} = 0.15A$$

$$V_1 = 22.2V \quad V_2 = 22.2V \quad V_3 = 77.8V$$

$$I_1 = 0.88A \quad I_2 = .15A \quad I_3 = 1.04A$$